

**IMPLEMENTATION OF MELODIC TONE
GENERATOR USING IC555**



ECB1204-ANALOG INTEGRATED CIRCUIT

A PROJECT REPORT

Submitted by

BALAJI K

KANNAN M

KARTHIK S

in partial fulfillment for the award of the degree

of

BACHELOR OF ENGINEERING

in

ELECTRONICS AND COMMUNICATION ENGINEERING

K.RAMAKRISHNAN COLLEGE OF TECHNOLOGY

(An Autonomous Institution, Affiliated to Anna University Chennai and Approved by AICTE, New Delhi)

SAMAYAPURAM, TIRUCHIRAPPALLI – 621 112

DECEMBER, 2024

**K. RAMAKRISHNAN COLLEGE OF TECHNOLOGY
(AUTONOMOUS)
SAMAYAPURAM, TIRUCHIRAPPALLI– 621 112**

BONAFIDE CERTIFICATE

Certified that this project report titled “IMPLEMENTATION OF MELODIC TONE GENERATOR USING IC555” is the bonafide work of **BALAJI K (2303811710621014), KANNAN M (2303811710621050), KARTHIK S (2303811710621051)** who carried out the project under my supervision. Certified further, that to the best of my knowledge the work reported herein does not form part of any other project report or dissertation on the basis of which a degree or award was conferred on an earlier occasion on this or any other candidate.

SIGNATURE

Dr. S. SYEDAKBAR, M.E., Ph.D.,

HEAD OF THE DEPARTMENT

Assistant Professor

Department of Electronics and
Communication Engineering

K Ramakrishnan College of Technology
(Autonomous)

Samayapuram – 621 112

SIGNATURE

Mr. A. PARTHIBARAJ, M.E., (Ph.D).,

SUPERVISOR

Assistant Professor

Department of Electronics and
Communication Engineering

K Ramakrishnan College of Technology
(Autonomous)

Samayapuram – 621 112

Submitted for the viva-voce examination held on

INTERNAL EXAMINER

EXTERNAL EXAMINER

DECLARATION

We jointly declare that the project report on **“IMPLEMENTATION OF MELODIC TONE GENERATOR USING IC555”** is the result of original work done by us and best of our knowledge, similar work has not been submitted to **“ANNA UNIVERSITY CHENNAI”** for the requirement of Degree of **BACHELOR OF ENGINEERING**. This project report is submitted on the partial fulfillment of the requirement of the award of Degree of **BACHELOR OF ENGINEERING**.

SIGNATURE

BALAJI K

KANNAN M

KARTHIK S

Place : Samayapuram

Date :

ACKNOWLEDGEMENT

It is with great pride that we express our gratitude and in-debt to our institution “**K. Ramakrishnan College of Technology (Autonomous)**”, for providing us with the opportunity to do this project.

We are glad to credit honorable and admirable chairman **Dr. K. RAMAKRISHNAN, B.E.**, for having provided the facilities during the course of our study in college.

We would like to express our sincere thanks to our beloved Executive Director **Dr. S. KUPPUSAMY, MBA, Ph.D.**, for forwarding our project and offering adequate duration in completing our project.

We would like to thank **Dr. N. VASUDEVAN, M.Tech., Ph.D.**, Principal, who gave opportunity to frame the project with full satisfaction.

We whole heartedly thank **Dr. S. SYEDAKBAR, M.E., Ph.D.**, Head of the Department, Department of Electronics and Communication Engineering for providing his encouragement in pursuing this project.

We express our deep and sincere gratitude to our project guide, **Mr.A.PARTHIBARAJ, M.E., (Ph.D)**, Assistant Professor, Department of Electronics and Communication Engineering, for his incalculable suggestions, creativity, assistance and patience which motivated us to carry out this project.

We wish to express my special thanks to the officials and Lab Technicians of our departments .

TABLE OF CONTENTS

CHAPTER	TITLE	PAGE NO
	PROBLEM STATEMENT	1
1	1.1 CUSTOMIZATION AND VERSATILITY	1
	1.2 LIMITATIONS IN SOUND COMPLEXITY	2
	1.3 PORTABILITY AND COMPACT DESIGN	2
	1.4 EDUCATIONAL VALUE	2
	1.5 BACKGROUND OF THE WORK	3
2	DESIGN PROCEDURE	4
	2.1 CIRCUIT DESIGN	4
	2.2 WORKING PRINCIPLE	6
	2.3 DESIGN&PROCEDURE	7
3	COST OF THE COMPONENTS	8
	3.1 COMPONENT BILL	9
4	RESULT AND DISCUSS	10
	4.1 WORKING MODEL	10
	4.2 FUNCTIONALITY	11
	4.3 RESULT ANALYSIS	12
	4.4 CONCLUSION	13

CHAPTER 1

PROBLEM STATEMENT

In the melodic tone generator sound based devices play a vital role in communication, entertainment, and various alarm systems. A melodic tone generator is an essential component in numerous applications such as toys, doorbells, alert systems, and musical devices. Designing an efficient and cost-effective melodic tone generator using an IC 555 timer presents a unique challenge due to its limited features and inherent design complexities. The goal is to develop a simple, reliable, and low-cost circuit capable of producing a range of tones with varying frequencies and melodic patterns while demonstrating the versatility of the IC 555 timer in monostable and astable configurations.

The primary challenge is to effectively utilize the IC 555 timer to produce controlled frequencies that mimic musical notes while ensuring the circuit is compact and energy-efficient. Additionally, integrating control mechanisms to generate varying melodies, managing frequency accuracy, and achieving desirable output volume add to the complexity of the design. Addressing these challenges through a practical and optimized solution can provide an affordable alternative to commercial tone generators for educational and small-scale applications.

The proposed system is designed to address specific problems:

1.1 CUSTOMIZATION AND VERSATILITY

Unlike fixed-frequency tone generators, this system offers customization by changing resistor and capacitor values, allowing users to create different frequencies and melodies. This flexibility is ideal for applications like musical toys, alarms, and educational tools.

1.2 LIMITATIONS IN SOUND COMPLEXITY:

Though simple and affordable, the system can only generate basic tones (square waves) and lacks the capability to produce complex, polyphonic sounds. It is most effective for projects where simple melodies are sufficient, such as in toy systems and low-cost alarms.

1.3 PORTABILITY AND COMPACT DESIGN:

The system's small form factor and battery-powered operation make it highly portable and ideal for integration into various devices. Its compact design ensures that it can be used in small electronic projects and devices without adding bulk or complexity.

1.4 EDUCATIONAL VALUE:

This system serves as a great educational tool to teach basic electronics concepts, such as oscillators, timing circuits, and sound-generation. It helps students and hobbyists gain hands-on experience with an essential IC like the 555 timer.

The melodic tone generator system using the IC 555 timer also has certain limitations, such as its inability to produce complex or polyphonic sounds and the restriction to basic square wave tones. Additionally, the frequency range is determined by the RC values, limiting the tonal variety. These limitations make it more suitable for small-scale projects where simplicity, low cost, and ease of implementation are prioritized over complex sound generation.

This project aims to demonstrate the practicality and effectiveness of a simple, low-cost tone generator, highlighting its advantages, addressing its limitations, and exploring its potential applications in educational tools, toys, alarms, and other sound-based devices.

1.5 BACKGROUND OF THE WORK:

The concept of sound generation in electronics dates back to the early days of circuit design, where oscillators were used to create audio signals for various applications. One of the most fundamental components in sound generation is the IC 555 timer, an integrated circuit that can be configured in several modes to generate accurate frequency signals. In its astable mode, the 555 timer is commonly used to produce square wave outputs, which are easily converted into sound when connected to a speaker. This makes the IC 555 a popular choice for tone generation applications due to its simplicity, affordability, and versatility.

Historically, tone generators were often large, expensive devices, typically used in professional equipment or complex systems. However, as technology advanced, the ability to create sound-producing circuits became more accessible. The 555 timer-based tone generator is an example of how a low-cost, compact solution can replace larger, more complicated systems. Over time, hobbyists and educators embraced the IC 555 timer for its ease of use in small-scale projects, offering a great introduction to basic electronics principles such as frequency generation, oscillation, and sound synthesis.

Despite its simplicity, the IC 555 timer is powerful enough to serve a wide range of applications. By adjusting external components like resistors and capacitors, users can modify the frequency and behavior of the tone generator.

This background highlights the importance and versatility of the IC 555 timer in sound generation, emphasizing its role in creating affordable, reliable, and educational solutions. As technology continues to evolve, the system can be further enhanced to address its limitations and expand its applications.

The system's adaptability, combined with its ease of implementation and low cost, makes it an ideal choice for a variety of applications. The IC 555 timer-based tone generator has proven itself as a practical solution in modern-day electronics.

CHAPTER 2

DESIGN PROCEDURE

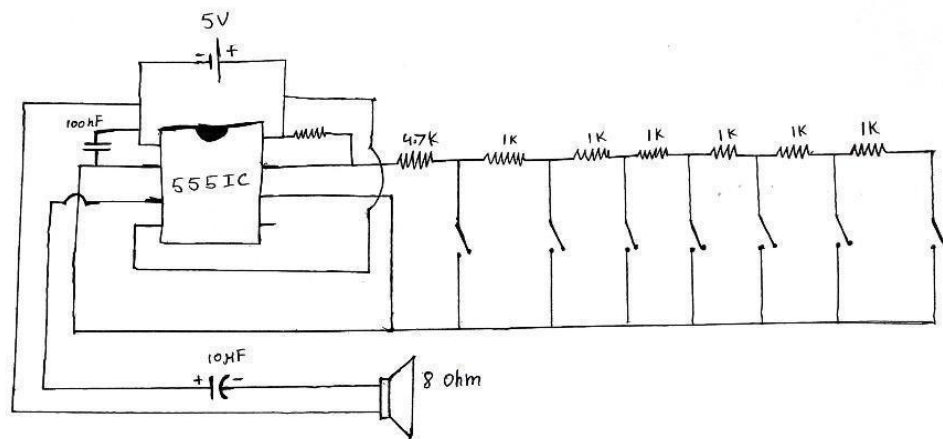


Fig:2.1 Circuit Diagram Melodic Tone Generator

2.1 CIRCUIT DESIGN:

The circuit is divided into five main components. They are used IC555 timer , 4.7K Ω & 1K Ω resistor , buzzer , push switch , 100 μ F & 100nF capacitor above the figure2.1 respresented.

2.1.1 IC 555 Timer:

Acts as the core of the tone generator circuit.It operates in astable mode to generate a continuous square wave signal, which determines the tone frequency.The frequency of oscillation depends on the connected resistors and capacitors. This signal is later used to drive the speaker, creating audible tones.

2.1.2 Resistor1 k Ω :

Sets the time constant for the RC network in conjunction with the capacitor. In a stable configuration, the 4.7k Ω & 1 k Ω resistor typically determines the charge or discharge time of the capacitor, affecting the frequency of the generated tone.

2.1.3 Push Switch:

Allows user interaction by activating or altering the circuit. When pressed, it either completes the circuit or switches between different resistors or capacitors, changing the frequency of the output tone. It can also be used to enable/disable the circuit.

2.1.4 Buzzer:

Converts the electrical signal generated by the IC 555 timer into audible sound. The buzzer is directly driven by the output pin of the IC 555 or through a transistor (if amplification is required). The quality and volume of the sound depend on the strength of the output signal.

2.1.5 Capacitor100 nF:

Used in the RC network to control the oscillation frequency of the IC 555. It works with the resistors to determine the frequency (pitch) of the generated tone. Likely placed at the power supply pins of the IC 555 to stabilize the voltage by filtering out noise. In some designs, it might also be used to smooth the output signal before it drives the speaker.

2.1.6 Resistor4.7k Ω :

Similar to the 1 k Ω resistor, it forms part of the RC network. It helps fine-tune the charge/discharge time of the capacitor and hence the frequency of the output. A higher resistor value will result in a lower frequency (deeper tone), and a lower value will result in a higher frequency (higher pitch).

2.1.7 Capacitor 100 μ F:

Used for decoupling or as a coupling capacitor. Likely placed at the power supply pins of the IC 555 to stabilize the voltage by filtering out noise. In some designs, it might also be used to smooth the output signal before it drives the speaker.

2.2 WORKING PRINCIPLE:

The working principle of the melodic tone generator using an IC 555 timer revolves around the concept of generating a continuous square wave signal, which is then converted into an audible sound by a connected speaker.

The IC 555 timer is configured in astable mode, meaning it continuously oscillates between its high and low states without the need for an external trigger. This oscillation is controlled by the external components, specifically resistors and capacitors, which set the timing interval for how long the output stays in its high or low state. As a result, the 555 timer produces a periodic signal that alternates between voltage levels at a fixed frequency, which corresponds to the pitch of the tone.

The frequency of the oscillation, and therefore the pitch of the generated tone, depends on the RC time constant (resistor and capacitor values) in the circuit. The 555 timer's duty cycle is primarily determined by the resistors (e.g., 1 k Ω and 4.7 k Ω) and capacitors (e.g., 100 nF) connected to it. The combination of these components dictates how quickly the capacitor charges and discharges, which in turn affects how quickly the timer switches its output.

Finally, the generated square wave signal from the 555 timer is fed to a speaker. The square wave alternates between high and low voltages, causing the speaker's diaphragm to vibrate, producing sound waves that we hear as tone or melody.

The speaker, typically an 8-ohm speaker, converts the electrical oscillations into mechanical vibrations at the set frequency. The resulting sound can be used for a variety of applications, such as creating alarm sounds, musical tones, or notification signals.

2.3 DESIGN&PROCEDURE:

WHERE

$$T=1.1RC ,$$

$$T=100\text{ms} ,$$

$$R=1\text{K}\Omega$$

$$R=100/1.1C \quad \dots(1)$$

$$C=100/1.1R \quad \dots(2)$$

$$=100/1.1$$

$$=90$$

$$\Rightarrow 90 \approx 100\mu\text{F}$$

2.3.1 EXPLANATION:

The design and procedure involve determining the capacitor value required for a circuit with a given time constant of 100 ms and a resistor of 1 k Ω . Using the formula , it is rearranged to . Substituting and , the calculation gives , which is rounded to the nearest standard value of . This capacitor value ensures the circuit operates at the desired time constant, suitable for applications like sound generation or alarms using an 8-ohm speaker.

CHAPTER 3

COST OF COMPONENTS

COMPONENT	QUANTITY	COST (APPROX.)
100 nF Capacitor	1	3
Push Button	7	21
Buzzer	1	20
9V Battery	1	20
IC 555 TIMER	1	20
1 k Ω Resistor	1	14
4.7k Ω Resistor	7	2
100 μ F Capacitor	1	3
Connecting Wires	As Required	10
Breadboard	1	90

The cost of the component were attached in Fig:3.1 component bill.They are used five components are buzzer , push button , resistor , Ic 555 timer , capacitor , connecting wires and breadboard

3.1 COMPONENT BILL:

ॐ
MEMO

தேதி: 21/11/24

Sundry	(8)	24
IC	(2)	40
Buzna	(1)	20
Pf	(5)	15
Cust	(3)	15
Rev	(12)	26
		140

அனைத்து டி வி க்கும் ரிமோட் கிடைக்கும்.

திருப்பதி எலக்ட்ரானிக்ஸ்
1647, தெற்கு வீதி. தஞ்சாவூர்.
Ph: 98056379931
விற்பனை பொருள் திரும்ப பெறப்படமாட்டாது.
No Return No Guaranty

Fig:3.1 component bill

CHAPTER 4

RESULT AND DISCUSSION

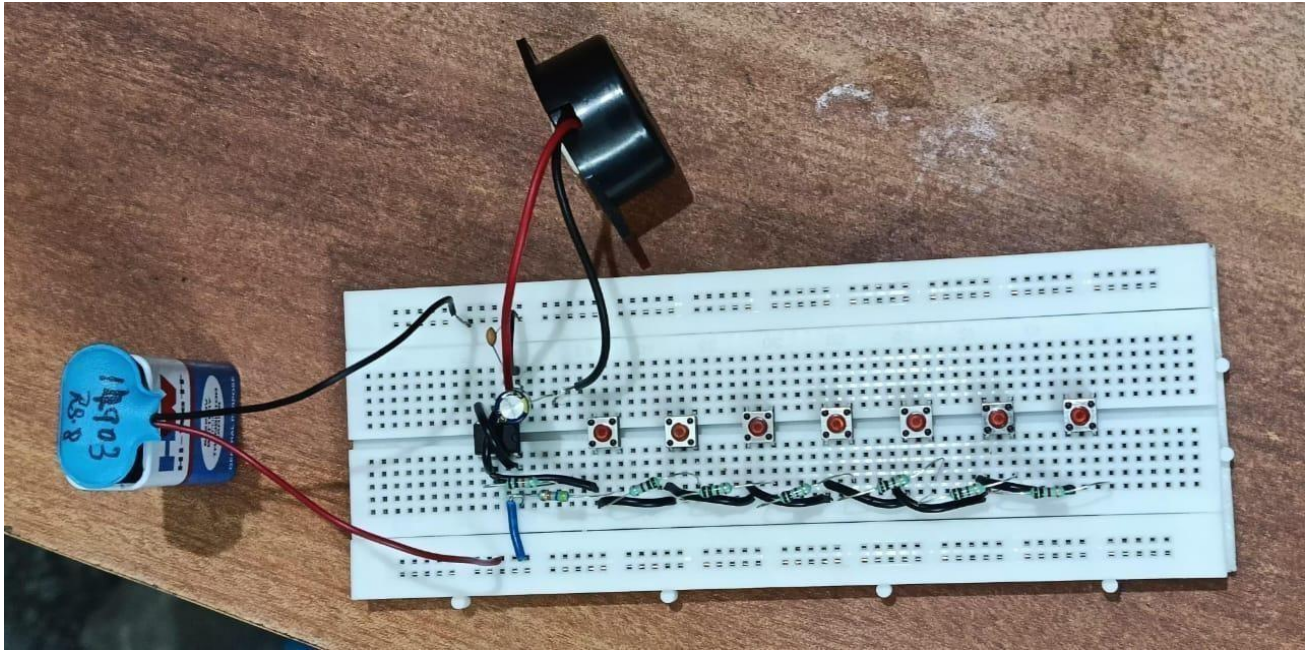


Fig:4.1 Circuit Diagram Melodic Tone Generator

The melodic tone generator using ic555 was successfully implemented and tested. The key observations and results are as follows:

4.1 WORKING MODEL:

The working model of the melodic tone generator consists of the following components and configuration. IC 555 Timer Configured in astable mode to generate a continuous square wave signal. RC Network Resistors and capacitors connected to the timer determine the oscillation frequency. Power Supply A 9V battery provides portability and ensures the circuit operates without reliance on external power. Speaker An 8-ohm speaker converts the electrical signals into sound waves, producing audible tones.

Optional Features Push-button switches or potentiometers can be added for real-time frequency adjustments or to cycle through different tones. During operation, the timer continuously oscillates, generating a square wave signal fed to the speaker. The RC network allows frequency customization, and the output is stable and reliable, making it suitable for various applications.

4.2 FUNCTIONALITY

The system generates consistent tones using the IC 555 timer in astable mode. Frequency is controlled by an RC network, allowing tone customization. The output square wave reliably drives an 8-ohm speaker for sound production.

4.2.1 ADVANTAGE:

Simple circuit design with readily available and inexpensive components. Portable and energy-efficient, operating on a 9V battery. Customizable frequency range enables a variety of tones. Easy to assemble and suitable for beginners and hobbyists.

4.2.2 LIMITATION:

Can only produce basic square wave tones, limiting sound complexity. Limited frequency range based on the RC network used. Output sound quality is restricted by the basic 8-ohm speaker. Not suitable for advanced applications requiring polyphonic or high-quality sound.

4.2.3 APPLICATION:

Used in low-cost devices like toys, alarms, and doorbells. Serves as an educational tool for learning basic electronics concepts. Useful in DIY projects for generating simple sound effects or melodies. Can act as a sound notifier in small-scale systems or gadgets.

4.2.4 FUTURE ENHANCEMENT:

Integration of microcontrollers for more complex sound patterns and melodies. Addition of amplifiers to improve sound quality and volume. Implementation of digital control for precise frequency adjustments. Expansion to include multiple speakers for polyphonic sound production.

4.3 RESULT ANALYSIS:

The melodic tone generator system using the IC 555 timer was successfully designed, implemented, and tested. Key observations include: Frequency Control, Sound Output, Ease of Operation, Limitations.

4.3.1 Frequency Control:

The system reliably produced square wave tones, with frequencies determined by the RC network. Adjustments to resistor and capacitor values effectively changed the tone.

4.3.2 Sound Output:

The 8-ohm speaker converted the square wave signal into audible sound with sufficient volume for small-scale applications like alarms or toys.

4.3.3 Ease of Operation:

The circuit demonstrated simple and reliable operation, with minimal need for adjustments during testing.

4.3.4 Limitations:

The system was unable to produce complex or polyphonic tones, and the sound quality was limited by the basic speaker and the square wave nature of the output.

4.4 CONCLUSION:

The project successfully demonstrated a simple, cost-effective method for generating tones using an IC 555 timer. The system is easy to design, implement, and customize, making it ideal for educational purposes, DIY projects, and low-cost applications like toys, alarms, and doorbells. While the system is limited to basic square wave tones, its simplicity and versatility provide a strong foundation for further enhancement. Future developments could include adding features like polyphonic capabilities, digital control, or amplifiers to expand its applications. Overall, the project highlights the practicality of the IC 555 timer for sound generation, balancing simplicity with functionality.

